

Experiment # 8  
Registers and Register Banks


**Objective:** Creating registers and register banks in VHDL.

**Prelab:** Please turn in the following parts at the **beginning of lab hour**.

Parts: 1A , 2A and 2A.a.

**Background:**

A register is a string of flip-flops all having the same clock line.

 

**Figure 8-1: Edge Triggered 4 Bit Register**

When the clock line goes from low to high the input to the flip-flop is transferred to the output. Circuit diagram in figure 1 is a collection of positive edge triggered flip-flops because the outputs get updated on a low to high transition of the clock line. Negative edge triggered flip-flop can be built by making the output change on a high to low transition of the clock.

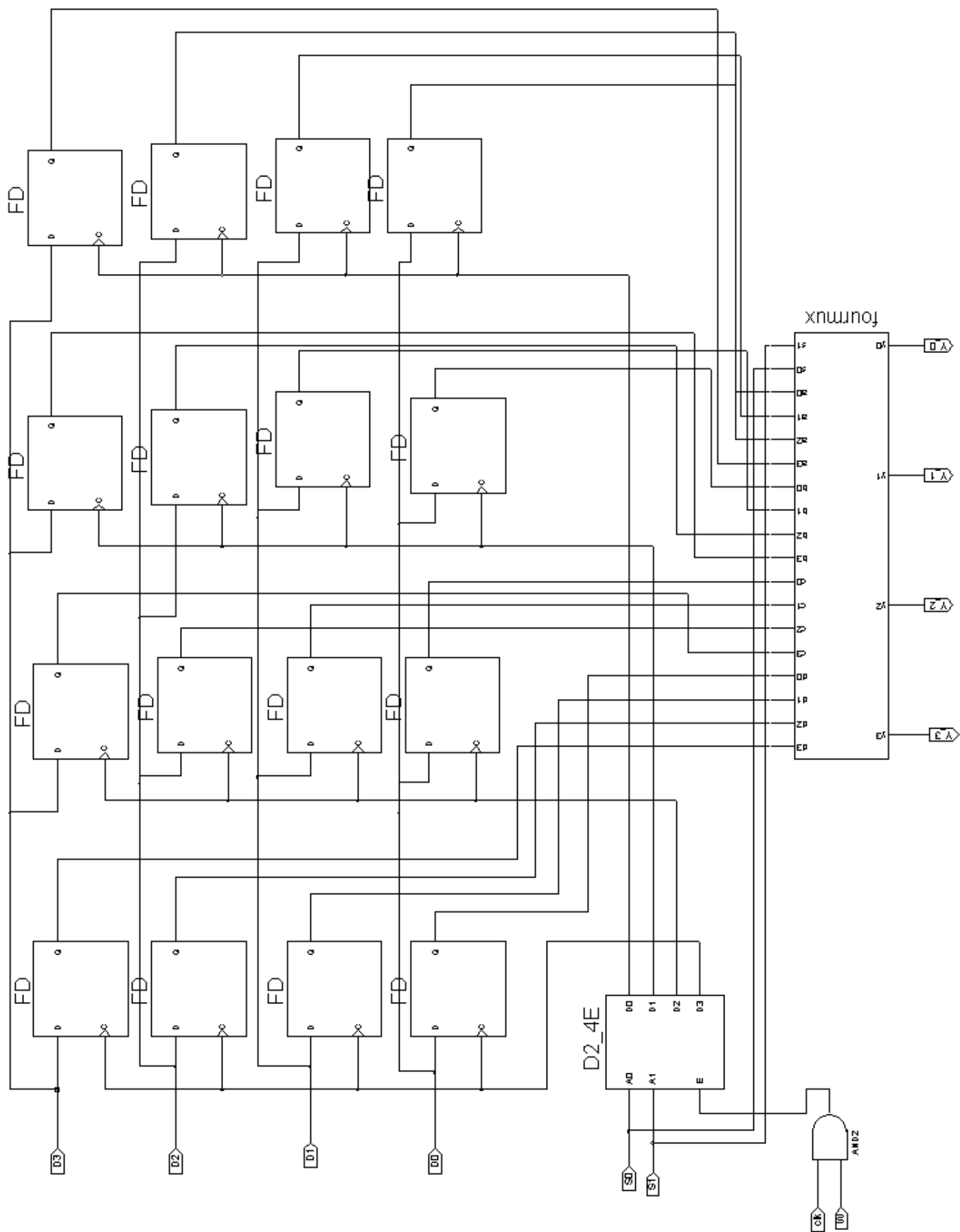


Figure 8-2: 4x4Bit Register Bank

A register bank is a set of address selectable registers.

Study of Figure 8-2 will show that when the input  $W = 1$ , the address lines ( $S_1S_0$ ) control which register gets updated on the low to high transition of the clock line. Study will also show the address lines ( $S_1S_0$ ) are used to control which register's output is routed to the output lines.

**Design:**

- 1) **A)** Write a VHDL description to implement a 4-bit positive edge triggered register. **Turn in a hard copy as prelab.**

**B)** Compile and simulate the code for selected input combinations.

(For simulation : For clock input of your register, assign 4ns clock period. For the flip-flop inputs, force the following combinations and run 8ns for each combination.  
0000, 0010 1010, 1100, 0011.

**NOTE :** Since the clock of the flip-flops will be driven directly by a regular I/O pin ( not by GCK pins of the FPGA ) , there would be a mapping error during implementing the design. The compiler adds an IBUFG buffer to the clock input, as a result the clock cannot be connected to a regular I/O pin. In order to change the error message to a warning, and to allow connection of the clock to an I/O pin, the following line should be added to the .ucf file. The following statement should be added after I/O planning step and all pin assignments. ( Assign one of the switches to your clock signal. )

NET "XXXXXX" CLOCK\_DEDICATED\_ROUTE = "FALSE";  
XXXXXX should be replaced by the clock assignment given your VHDL file.

**C)** Download and test it on the board.

- 2) **A)** Write a VHDL description to implement the 4x4Bit Register Bank of Figure 2. **Turn in a hard copy as prelab.**

**a.** Write a VHDL description for a 2 to 4 decoder with enable. (Use it as a component.) **Turn in a hard copy as prelab.**  
Compile and simulate the code for all input combinations.

**b.** Use 4 copies of 4-bit register of part one. (Components)

**c.** Use a copy of multiplexer designed in Lab 7. (Component).

**d.** Add the necessary code to complete the source code.

**B)** Compile and simulate the code for the following input combinations.

(  $W$  and ( $S_1S_0$ ) cannot change at the same time and  $W$  has to be equal to 0 when ( $S_1S_0$ ) change.)

Assign 4ns period for clk with **FALLING** edge.

$W = 0$	run 8ns
$(W = 0) S_1S_0 = 00 \quad D_3D_2 D_1D_0 = 0011$	run 8ns
$W = 1$	run 8ns
$W = 0$	run 8ns

(W = 0) S <sub>1</sub> S <sub>0</sub> = 01	D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub> = 1010	run 8ns
W = 1		run 8ns
W = 0		run 8ns
(W = 0) S <sub>1</sub> S <sub>0</sub> = 10	D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub> = 0101	run 8ns
W = 1		run 8ns
W = 0		run 8ns
(W = 0) S <sub>1</sub> S <sub>0</sub> = 11	D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub> = 1100	run 8ns
W = 1		run 8ns
W = 0		run 8ns
(W = 0) S <sub>1</sub> S <sub>0</sub> = 00	run 8ns	Check the outputs Y <sub>3</sub> through Y <sub>0</sub>
(W = 0) S <sub>1</sub> S <sub>0</sub> = 01	run 8ns	Check the outputs Y <sub>3</sub> through Y <sub>0</sub>
(W = 0) S <sub>1</sub> S <sub>0</sub> = 10	run 8ns	Check the outputs Y <sub>3</sub> through Y <sub>0</sub>
(W = 0) S <sub>1</sub> S <sub>0</sub> = 11	run 8ns	Check the outputs Y <sub>3</sub> through Y <sub>0</sub>

C) Download and test it on the board.

**All final VHDL files and simulation results of each part should be included in the report.**